

- [Home](#)
- [Forums](#)
- [Datasheets](#)
- [Lab Manual](#)
- [Testing Components](#)
- [Buy Project Kits](#)

# [Electronic Circuits and Diagram-Electronics Projects and Design](#)

Google™ Custom Search

AdChoices 

[▶ 16X2 LCD Display](#)

[▶ Circuit Diagram](#)

[▶ Arduino TFT LCD](#)

[▶ LCD Datasheet](#)

## Interfacing 16×2 LCD with 8051

[admin](#)

June - 1 - 2012

[23 Comments](#)



LCD display is an inevitable part in almost all embedded projects and this article is about interfacing 16×2 LCD with 8051 microcontroller. Many guys find it hard to interface LCD module with the 8051 but the fact is that if you learn it properly, its a very easy job and by knowing it you can easily design embedded projects like digital voltmeter / ammeter, digital clock, home automation displays, status indicator display, digital code locks, digital speedometer/ odometer, display for music players etc etc. Thoroughly going through this article will make you able to display any text (including the extended characters) on any part of the 16×2 display screen. In order to understand the interfacing first you have to know about the 16×2 LCD module.

### 16×2 LCD module.

16×2 LCD module is a very common type of LCD module that is used in 8051 based embedded projects. It consists of 16 rows and 2 columns of 5×7 or 5×8 LCD dot matrices. The module were are talking about here is type number JHD162A which is a very popular one . It is available in a 16 pin package with back light ,contrast adjustment function and each dot matrix has 5×8 dot resolution. The pin numbers, their name and corresponding functions are shown in the table below.

Pin No:	Name	Function
---------	------	----------

1	VSS	This pin must be connected to the ground
2	VCC	Positive supply voltage pin (5V DC)
3	VEE	Contrast adjustment
4	RS	Register selection
5	R/W	Read or write
6	E	Enable
7	DB0	Data
8	DB1	Data
9	DB2	Data
10	DB3	Data
11	DB4	Data
12	DB5	Data
13	DB6	Data
14	DB7	Data
15	LED+	Back light LED+
16	LED-	Back light LED-

VEE pin is meant for adjusting the contrast of the LCD display and the contrast can be adjusted by varying the voltage at this pin. This is done by connecting one end of a POT to the Vcc (5V), other end to the Ground and connecting the center terminal (wiper) of the POT to the VEE pin. See the circuit diagram for better understanding.

The JHD162A has two built in registers namely data register and command register. Data register is for placing the data to be displayed , and the command register is to place the commands. The 16×2 LCD module has a set of commands each meant for doing a particular job with the display. We will discuss in detail about the commands later. High logic at the RS pin will select the data register and Low logic at the RS pin will select the command register. If we make the RS pin high and the put a data in the 8 bit data line (DB0 to DB7) , the LCD module will recognize it as a data to be displayed . If we make RS pin low and put a data on the data line, the module will recognize it as a command.

R/W pin is meant for selecting between read and write modes. High level at this pin enables read mode and low level at this pin enables write mode.

E pin is for enabling the module. A high to low transition at this pin will enable the module.

DB0 to DB7 are the data pins. The data to be displayed and the command instructions are placed on these pins.

LED+ is the anode of the back light LED and this pin must be connected to Vcc through a suitable series current limiting resistor. LED- is the cathode of the back light LED and this pin must be connected to ground.

### **16×2 LCD module commands.**

16×2 LCD module has a set of preset command instructions. Each command will make the module to do a particular task. The commonly used commands and their

function are given in the table below.

Command	Function
0F	LCD ON, Cursor ON, Cursor blinking ON
01	Clear screen
2	Return home
4	Decrement cursor
06	Increment cursor
E	Display ON ,Cursor ON
80	Force cursor to the beginning of 1 <sup>st</sup> line
C0	Force cursor to the beginning of 2 <sup>nd</sup> line
38	Use 2 lines and 5×7 matrix
83	Cursor line 1 position 3
3C	Activate second line
0C3	Jump to second line, position3
OC1	Jump to second line, position1

### **LCD initialization.**

The steps that has to be done for initializing the LCD display is given below and these steps are common for almost all applications.


- Send 38H to the 8 bit data line for initialization
- Send 0FH for making LCD ON, cursor ON and cursor blinking ON.
- Send 06H for incrementing cursor position.
- Send 01H for clearing the display and return the cursor.

### **Sending data to the LCD.**

The steps for sending data to the LCD module is given below. I have already said that the LCD module has pins namely RS, R/W and E. It is the logic state of these pins that make the module to determine whether a given data input is a command or data to be displayed.

- Make R/W low.
- Make RS=0 if data byte is a command and make RS=1 if the data byte is a data to be displayed.
- Place data byte on the data register.
- Pulse E from high to low.
- Repeat above steps for sending another data.

## Circuit diagram.

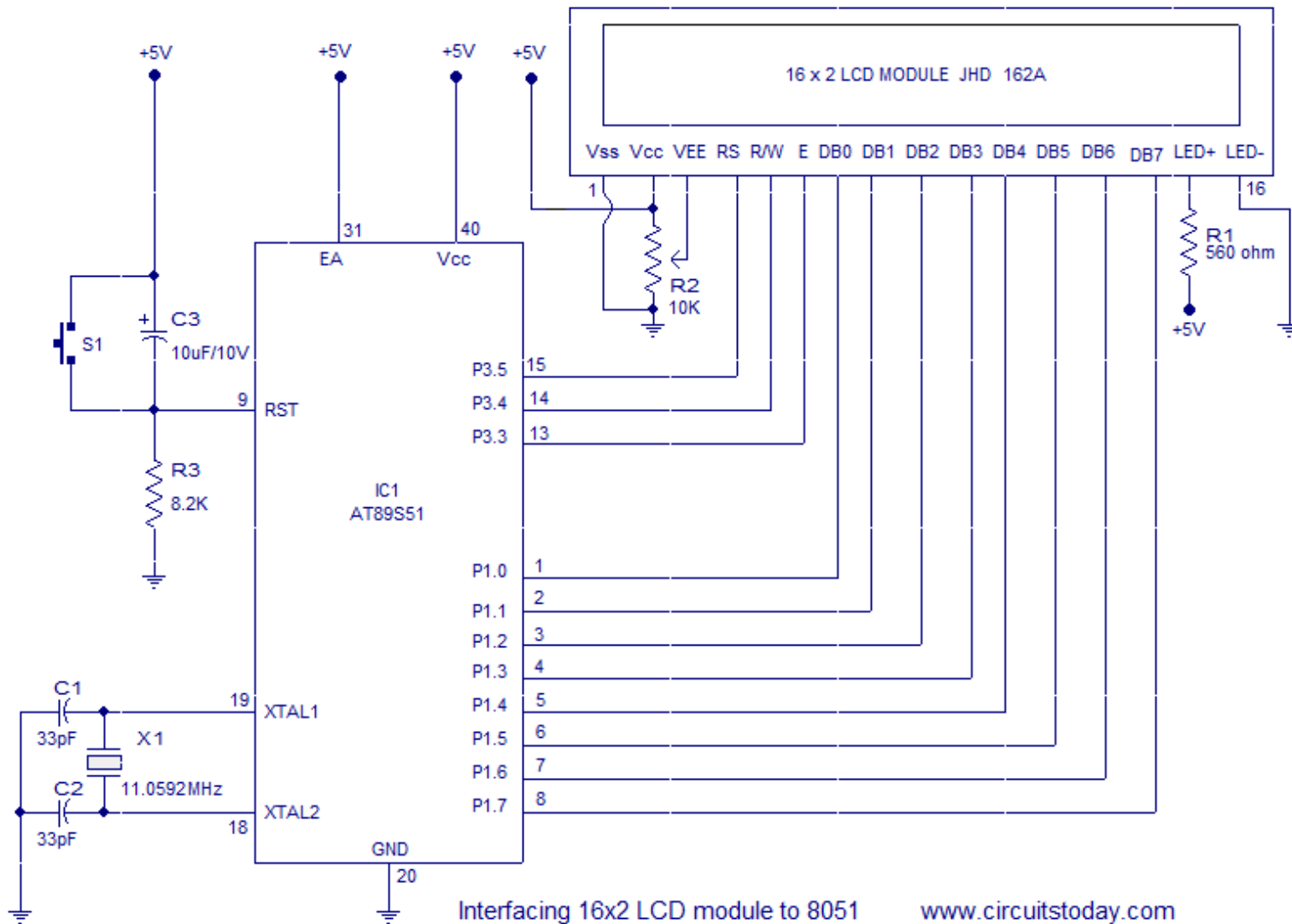

### Interfacing 16×2 LCD module to 8051

The circuit diagram given above shows how to interface a 16×2 LCD module with AT89S1 microcontroller. Capacitor C3, resistor R3 and push button switch S1 forms the reset circuitry. Ceramic capacitors C1,C2 and crystal X1 is related to the clock circuitry which produces the system clock frequency. P1.0 to P1.7 pins of the microcontroller is connected to the DB0 to DB7 pins of the module respectively and through this route the data goes to the LCD module. P3.3, P3.4 and P3.5

are connected to the E, R/W, RS pins of the microcontroller and through this route the control signals are transferred to the LCD module. Resistor R1 limits the current through the back light LED and so do the back light intensity. POT R2 is used for adjusting the contrast of the display.

## Program.

```
MOV A,#38H // Use 2 lines and 5x7 matrix
ACALL CMND
MOV A,#0FH // LCD ON, cursor ON, cursor blinking ON
ACALL CMND
MOV A,#01H //Clear screen
ACALL CMND
MOV A,#06H //Increment cursor
ACALL CMND
MOV A,#82H //Cursor line one , position 2
ACALL CMND
MOV A,#3CH //Activate second line
ACALL CMND
MOV A,#49D
ACALL DISP
MOV A,#54D
ACALL DISP
MOV A,#88D
ACALL DISP
MOV A,#50D
ACALL DISP
MOV A,#32D
ACALL DISP
MOV A,#76D
ACALL DISP
MOV A,#67D
ACALL DISP
MOV A,#68D
ACALL DISP

MOV A,#0C1H //Jump to second line, position 1
ACALL CMND

MOV A,#67D
ACALL DISP
MOV A,#73D
ACALL DISP
MOV A,#82D
ACALL DISP
MOV A,#67D
ACALL DISP
MOV A,#85D
ACALL DISP
```

```
MOV A,#73D
ACALL DISP
MOV A,#84D
ACALL DISP
MOV A,#83D
ACALL DISP
MOV A,#84D
ACALL DISP
MOV A,#79D
ACALL DISP
MOV A,#68D
ACALL DISP
MOV A,#65D
ACALL DISP
MOV A,#89D
ACALL DISP
```

```
HERE: SJMP HERE
```

```
CMND: MOV P1,A
CLR P3.5
CLR P3.4
SETB P3.3
CLR P3.3
ACALL DELY
RET
```

```
DISP:MOV P1,A
SETB P3.5
CLR P3.4
SETB P3.3
CLR P3.3
ACALL DELY
RET
```

```
DELY: CLR P3.3
CLR P3.5
SETB P3.4
MOV P1,#0FFh
SETB P3.3
MOV A,P1
JB ACC.7,DELY
```

```
CLR P3.3
CLR P3.4
RET
```

```
END
```

Subroutine CMND sets the logic of the RS, R/W, E pins of the LCD module so that the module recognizes the input data ( given to DB0 to DB7) as a command.

Subroutine DISP sets the logic of the RS, R/W, E pins of the module so that the module recognizes the input data as a data to be displayed .

## TOPWAY LCD Module



topwaydisplay.com

Industrial LCM Design &  
Manufactory STN, FSTN Graphic  
Character Module

### You may also like:

- [8051 Timers and Counters](#)
- [Interfacing dot matrix LED display to 8051](#)
- [Interfacing hex keypad to 8051](#)
- [Delay using 8051 timer](#)
- [Software delay routine in 8051 microcontroller](#)

### We recommend:

- [Three phase auto changer circuit](#)
- [PROCEDURE TO USE MPLAB SIM](#)
- [Class B power amplifier](#)
- [Flashing battery monitor](#)
- [Lamp flasher circuit](#)

Search

Google™ Custom Search

Posted in [8051](#)

Tags: [interfacing LCD with 8051](#)

## Leave a Reply

Name (required)

Mail (will not be published) (required)

Website

Submit Comment

## 23 Responses to “Interfacing 16×2 LCD with 8051”

- *Fajar* says:  
[November 4, 2014 at 12:57 am](#)

There is nothing appearing on lcd.Please help!

[Reply](#)

- *Mihir* says:  
[October 7, 2014 at 8:11 am](#)

Thankyou for taking the efforts!  
It works!

[Reply](#)

- *keith formosa* says:  
[January 14, 2014 at 8:59 am](#)



hi nothing is appearing on my lcd, circuit is ok and program is copied from yours.

[Reply](#)

- *swapnil* says:  
[January 13, 2014 at 10:06 pm](#)

can anybody send me program for resistance colour code calculator using microcontroller please send asm program

[Reply](#)

- *Benjamin* says:  
[November 17, 2013 at 8:37 am](#)

Could you explain me how DELY subroutine produces the delay?

```
DELY:
MOV P1,#0FFh
MOV A,P1
JB ACC.7,DELY <——
RET;
```

I mean, when the condition will be met if the program write a full-ones word at P1 every time?

Sorry for the question.

[Reply](#)

- *jojo* says:  
[August 19, 2013 at 8:21 am](#)

@ Vivek,

It means, if bit 7 of accumulator is SET (that is 1), then jump to the delay routing labelled DELY. I hope you understood 😊 Any more doubts ?

[Reply](#)

- *vivek dixit* says:  
[August 18, 2013 at 11:45 am](#)

what is this “JB ACC.7,DELY”? plz reply soon

[Reply](#)

- *Gowtham pavanaskar* says:  
[May 24, 2014 at 11:03 pm](#)

If the 7th bit of the accumulator is 1, then it jumps to DELY. Else it executes the next instruction

[Reply](#)

- *kp* says:  
[June 27, 2013 at 5:59 am](#)

esta muy completa a informacion!! muchas gracias

[Reply](#)

- *MAHESH* says:  
[March 2, 2013 at 6:20 am](#)

hi.

can anybody send me circuit and programming of sms based home appliance control system?

[Reply](#)

- *Payal Patel* says:  
[November 4, 2012 at 7:09 am](#)

Nice explanation...

[Reply](#)

- *MD ZIAUR RAHMAN* says:  
[September 27, 2012 at 8:32 am](#)

```
#include
#include"delay1sec.h"
#define lcd_dat P1
sbit rs=P3^0;
sbit rw=P3^1;
sbit en=P3^2;

void write_lcd(char);
void cmd_lcd(char);
void disp_lcd(char);
void init_lcd();
void str_lcd(char *s);
void int_lcd(unsigned int);
void float_lcd(float);

void write_lcd(char dat)
{
  lcd_dat=dat;
```

```

rw=0;
en=1; //for latching one byte info
en=0; //clear for latching next info
delay_ms(2);
}

void cmd_lcd(char cmd)
{
rs=0; //set cmd register
write_lcd(cmd);
}

void disp_lcd(char c)
{
rs=1; //set data register
write_lcd(c);
}

void init_lcd()
{
cmd_lcd(0x02); //return cursor home
cmd_lcd(0x38); //8bit mode of operation
cmd_lcd(0x0e); //display on cur off
cmd_lcd(0x01); //clr DDRAM (display data ram)
cmd_lcd(0x06); //shift cursor right after each character displayed
cmd_lcd(0x80); //begin disp from line 1 pos 0
}

void str_lcd(char *s)
{
while(*s)
disp_lcd(*s++);
}

/*
main()
{
init_lcd();
str_lcd("*****");
cmd_lcd(0xc0);
str_lcd("*****");
while(1);
}

```

```

*/

main()
{
unsigned char i;
init_lcd();

for(i=0;i<16;i++)

{
cmd_lcd(0x80+i);
str_lcd("WELCOME");
delay_ms(500);
cmd_lcd(0x01);
cmd_lcd(0x80);

}

}

```

#### [Reply](#)

- *vinay* says:  
[April 29, 2013 at 12:21 am](#)

i want lcd program in asm

#### [Reply](#)

- *riddhi* says:  
[October 6, 2013 at 11:17 pm](#)

Anybody can send me the programing for lcd interfacing with microcontroller and xbee s2

#### [Reply](#)

- *keith formosa* says:  
[January 14, 2014 at 8:51 am](#)

Hi I constructed the circuit exactly as it is on my simulator and just copied the program and nothing is appearing on the LCD

#### [Reply](#)

- *vivek* says:  
[September 26, 2012 at 10:18 am](#)

Sir,  
please try to think this circuit by IC ULN2003 at the place of transistors.

[Reply](#)

- *vinod* says:  
[August 9, 2012 at 9:37 am](#)

nice work, but please write the programme in embedded c

[Reply](#)

- *mg* says:  
[June 28, 2012 at 11:12 am](#)

nice post

[Reply](#)

- [KALPESH CHHABHAIYA](#) says:  
[June 3, 2012 at 11:28 pm](#)

nice work dude 😊

[Reply](#)

- *rowan walters* says:  
[June 3, 2012 at 1:55 am](#)

absolutely loved this

[Reply](#)

- *jojo* says:  
[June 3, 2012 at 7:04 am](#)

Thank you Rowan. Please try it. Comment if you come across any doubts.

[Reply](#)

- *Laxman* says:  
[November 23, 2012 at 2:32 am](#)

Real wonderful work.....

[Reply](#)

- *p* says:  
[September 10, 2014 at 9:57 am](#)

Pls provide alp programs for LCD interfacing

[Reply](#)



## Get Daily Updates via Email

20001 readers  
BY FEEDBURNER

## Latest Articles

- [IPCA Electronics Expo 2015 – Revolutionizing the Make in India campaign](#)
- [Interfacing pressure sensor to arduino](#)
- [We Are Launching An Online Store to Shop Electronic Kits,Boards and Components](#)
- [Digital Code Lock using Arduino with LCD Display and User Defined Password](#)
- [The Big List of Arduino Projects and Circuits](#)
- [Interfacing gyroscope to arduino](#)
- [LPG sensor using arduino](#)
- [OhmMeter using Arduino – with Auto Ranging Feature](#)
- [8051 Timers and Counters](#)
- [We are on all Social Media – Youtube Facebook Twitter LinkedIn and Slideshare](#)



# FREE PCB Design Software

## Categories

- [101-Announcements](#)
- [555 Timer IC](#)
- [8051](#)
- [8051 projects](#)
- [Amplifier Circuits](#)
- [Arduino](#)
- [Audio Circuits](#)
- [Automotive Circuits](#)
- [AVR](#)
- [Basic Electricity](#)
- [Basic Electronics](#)
- [Battery Circuits](#)
- [C plus plus](#)
- [C Programming](#)
- [Cable TV Circuits](#)
- [Camera Technology](#)
- [Clipping and Clamping Circuits](#)
- [Clocking & Timer Circuits](#)
- [Conversion Circuits](#)
- [Counter Circuits](#)
- [Counters](#)
- [Digital Electronics](#)
- [Education & Training](#)



- [Electronic Components](#)
- [Electronic Keys & Locks](#)
- [Electronics Books](#)
- [Electronics Jobs](#)
- [Embedded Systems](#)
- [Equipment Reviews](#)
- [Events](#)
- [Fan Circuits](#)
- [Filter Circuits](#)
- [Fire Alarm](#)
- [Fun & Game Circuits](#)
- [Gadget Reviews](#)
- [Ham Radio Circuits](#)
- [High Voltage Circuits](#)
- [History](#)
- [Home Circuits](#)
- [Industrial Circuits](#)
- [Instruments](#)
- [Integrated Circuits](#)
- [Inverters](#)
- [Lab Manuals](#)
- [LED related](#)
- [Light Related](#)
- [Lighting Circuits](#)
- [MATLAB](#)
- [Microcontrollers](#)
- [Mobile Phone Related](#)
- [Motor Related](#)
- [Nanotechnology](#)
- [Oscillators](#)
- [Peripheral Interface Controller \(PIC\)](#)
- [Power Controller Circuits](#)
- [Power Electronics](#)
- [Power Supplies](#)
- [Project Ideas](#)
- [Projects](#)
- [Proximity Detectors](#)
- [Radio Circuits](#)
- [Radio Transmitters](#)
- [Raspberry Pi](#)

- [Relays](#)
- [Remote Circuits](#)
- [Reviews](#)
- [Robotics](#)
- [RTOS](#)
- [Security & Safety](#)
- [Sensor Circuits](#)
- [Signal Conditioners](#)
- [Signal Generators](#)
- [Speed Controller Circuits](#)
- [State space analysis](#)
- [Switching Circuits](#)
- [Tech News](#)
- [Telephone Related](#)
- [Television Related](#)
- [Temperature Related](#)
- [Test & Measurement Circuits](#)
- [Testing Components](#)
- [Three phase circuits](#)
- [Timer Circuits](#)
- [Tone generator circuits](#)
- [Tools and Softwares](#)
- [Transmitters](#)
- [Tutorials](#)
- [UPS](#)
- [USB Circuits](#)
- [Videos](#)
- [VLSI](#)
- [Voltage Regulators](#)

**Like Us on Facebook**



## Recent Comments

- jojo on [4 Great Books to Learn Basic Electronics](#)
- tanishq mehta on [4 Great Books to Learn Basic Electronics](#)
- Jefferson Barrion on [150 Watt amplifier circuit](#)
- B.VIDHYA on [Electronics Mini projects](#)
- awais mughal on [Subwoofer filter](#)
- awais mughal on [Car subwoofer filter](#)
- jojo on [Simple Water Level Indicator](#)
- awais mughal on [2 x 32 Watts stereo amplifier](#)
- awais mughal on [2 x 32 Watts stereo amplifier](#)
- VAIBHAV on [24W amplifier using TDA1516](#)
- VIVEK VERMA on [24W amplifier using TDA1516](#)
- [sathiyan](#) on [Ultrasonic range finder using 8051](#)
- sandiya on [Simple Water Level Indicator](#)
- jojo on [Digital thermometer using arduino](#)
- Waleed on [Digital thermometer using arduino](#)

## Pages

- [About](#)
- [Advertise With Us](#)
- [Authors](#)

- [Buy Project Kits](#)
- [Datasheets](#)
- [Electronic Circuit Symbols](#)
- [Lab Manuals](#)
  - [Electronic Circuits Lab](#)
  - [Microcontroller lab](#)
  - [Microprocessor Lab](#)
- [Privacy Policy](#)
- [Project Contests](#)
- [Resistor Color Code Calculator](#)
- [Sitemap](#)
- [Testing Components](#)

## Popular Tags

[555 IC](#) [555 timer](#) [Audio Amplifier Circuits](#) [Audio circuits](#) [circuit design](#) [circuit diagram](#) [Electronic Circuits](#) [Electronic Components](#) [Electronic Instruments](#) [Filter Circuits](#) [History of Electronics](#) [hobby circuits](#) [hobby projects](#) [Home Circuits](#) [IC](#) [Integrated Circuits](#) [Most Popular Circuits](#) [Nanotechnology](#) [NE555 timer](#) [Oscillators](#) [PIC](#) [Power Supplies](#) [Radio Circuits](#) [SCR](#) [Simple Electronics Projects](#) [Tech News](#) [Thyristors](#) [Tutorials](#) [VLSI](#) [Voltage Regulators](#)

## Most Discussed

- [150 Watt amplifier circuit](#)
- [100 Watt sub woofer amplifier.](#)
- [Mains Operated LED Circuit](#)
- [Automatic LED Emergency Light-Modified Version](#)
- [2 km FM transmitter](#)
- [Suggest a Topic to Publish & Win a 8GB Pen Drive](#)
- [Automatic LED Emergency Light](#)

Copyright © 2007 - 2011 [Circuitstoday.com](#) Designed by [Web Design Cochin](#)

